

Section A

1. Since the source is symmetrical,  $V_L = \sqrt{3} \cdot 120 = 208 \text{ V}$ , and with the notation of Figure 1:

$$\begin{cases} \bar{V}_{L1} = 208 \angle -30^\circ \text{ V} = (180 - j104) \text{ V} \\ \bar{V}_{L2} = 208 \angle 90^\circ \text{ V} = j208 \text{ V} \\ \bar{V}_{L3} = 208 \angle -150^\circ \text{ V} = (-180 - j104) \text{ V} \end{cases}$$

2. Phase currents can be found using Ohm's Law:

$$\bar{I}_{P1} = \bar{V}_{L1} / 40 \angle 0^\circ = 5.2 \angle -30^\circ \text{ A} = (4.5 - j2.6) \text{ A}$$

$$\bar{I}_{P2} = \bar{V}_{L2} / 20 \angle -60^\circ = 10.4 \angle 150^\circ \text{ A} = (-9 + j5.2) \text{ A}$$

$$\bar{I}_{P3} = \bar{V}_{L3} / 15 \angle 45^\circ = 13.8 \angle -195^\circ \text{ A} = (-13.4 + j3.6) \text{ A}$$

3. Line currents can be found using KCL:

$$\bar{I}_{L1} = \bar{I}_{P1} - \bar{I}_{P3} = (17.9 - j6.2) \text{ A}$$

$$\bar{I}_{L2} = \bar{I}_{P2} - \bar{I}_{P1} = (-13.5 + j7.8) \text{ A}$$

$$\bar{I}_{L3} = \bar{I}_{P3} - \bar{I}_{P2} = (-4.4 - j1.6) \text{ A}$$

Note that:  $\bar{I}_{L1} + \bar{I}_{L2} + \bar{I}_{L3} \neq 0$  #

Section B

4. Reluctance in the airgap (with  $x = 3.5$  mm):

$$\mathcal{R}_1 = \frac{x}{\mu_0 A} = \frac{0.0035}{4 \cdot \pi \cdot 10^{-7} \cdot \pi \cdot 0.015^2} = 3,940,268 \frac{\text{At}}{\text{Wb}}$$

hence:  $L_1 = \frac{N^2}{\mathcal{R}_1} = \frac{4000^2}{\mathcal{R}_1} = 4.06 \text{ H}$

and the force is:  $f = \frac{1}{2} \frac{\mathcal{R}}{\pi x} i^2 = - \frac{1}{2} \frac{\mu_0 A N^2}{2x} i^2 = -0.5221 \text{ N}$

5. Reluctance in the airgap with  $x = 5$  mm:

$$\mathcal{R}_2 = \frac{x}{\mu_0 A} = \frac{0.005}{4 \cdot \pi \cdot 10^{-7} \cdot \pi \cdot 0.015^2} = 5,628,955 \frac{\text{At}}{\text{Wb}}$$

hence:  $L_2 = \frac{N^2}{\mathcal{R}_2} = \frac{4000^2}{\mathcal{R}_2} = 2.84 \text{ H}$

$$W_f(3.5 \text{ mm}) = \frac{1}{2} i^2 L_1 = 0.001827 \text{ J}$$


$$W_f(5 \text{ mm}) = \frac{1}{2} i^2 L_2 = 0.001279 \text{ J}$$

$$\Delta W_f = W_f(5 \text{ mm}) - W_f(3.5 \text{ mm}) = -0.000548 \text{ J}$$

#

Section C

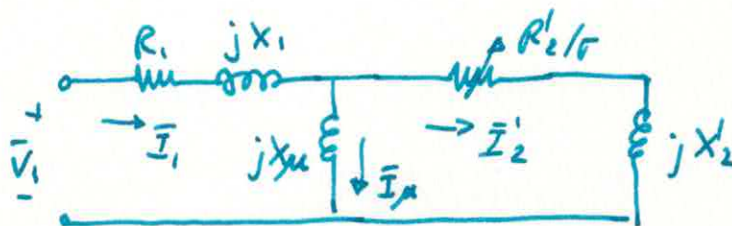6. Let assume the following equivalent circuit of the motor:



where  $X_{\mu} = 1/B_{\mu}$

The equivalent impedance of the circuit is:

$$\begin{aligned} \bar{z}_{eq} &= (R_1 + jX_1) + jX_{\mu} \parallel \overbrace{(R_2/s + jX_2)}^{R_F + jX_F} = \\ &= (9.40 + j4.64) \Omega = (10.5 \angle 26.3^\circ) \Omega \end{aligned}$$

Let  $\bar{V}_1 = 127 \angle 0^\circ \text{ V}$ , then:  $\bar{I}_1 = \frac{\bar{V}_1}{\bar{z}_{eq}} = 12.1 \angle -26.3^\circ \text{ A}$

$\Rightarrow \cos \phi_1 = \cos(-26.3^\circ) = 0.90$  (lagging)

7. The airgap power is  $P_{c1} = 3 R_2/s (I_2')^2 = 3 R_F I_1^2 = 3,920 \text{ W}$   
 Mechanical power  $P_m = (1 - \sigma) P_{c1} = 0.96 \cdot 3920 = 3760 \text{ W}$   
 Synchronous speed  $\omega_{c1} = 4\pi f/p = 188.5 \text{ rad/s}$   
 mechanical speed  $\omega_m = (1 - \sigma) \omega_{c1} = 181 \text{ rad/s}$   
 Mechanical torque  $T_m = P_m / \omega_m = 20.8 \text{ Nm}$  #

Section D

$$8. \quad V = \frac{4600}{\sqrt{3}} = 2,660 \text{ V} \quad \text{phase voltage}$$

$$I = \frac{1000 \cdot 10^3}{3V} = 125 \text{ A} \quad \text{current in each phase}$$

At unity power factor:

$$\begin{aligned} \bar{E} &= \bar{V} + IR_a + jIX_s \quad \text{where } \bar{V} = V \angle 0 \\ &= 2660 + 125 \cdot 2 + j125 \cdot 20 \\ &= 2,910 + j2500 \\ |E| &= 3,845 \text{ V} \end{aligned}$$

9. At 0.75 power factor lagging:

$$\begin{aligned} \bar{E} &= (V \cos \theta + IR_a) + j(V \sin \theta + IX_s) \\ &= (2,660 \cdot 0.75 + 125 \cdot 2) + j(2,660 \cdot 0.676 + 2500) \\ &= 2250 + j4270 \\ |E| &= 4,820 \text{ V} \end{aligned}$$

→ we have assumed  $\bar{V} = V \cos \theta + jV \sin \theta$  #

Section E

10. Let's use the single phase equivalent -

$$\text{Phase voltage: } E = 440/\sqrt{3} = 254 \text{ V}$$

$$\text{Current in the lighting load: } I_L = E/15\Omega = 16.9 \text{ A}$$

$$P_L = 3 E I_L = 3 \cdot 254 \cdot 16.9 = 12.9 \text{ kW}$$

11. Current in the motor:  $\bar{I}_M = \frac{E L_0}{10 + j5} = 22.68 \angle -26.57^\circ \text{ A}$   
 $= (20.28 - j10.14) \text{ A}$

$$P_M = 3 E \operatorname{Re}\{\bar{I}_M\} = 3 \cdot 254 \cdot 20.28 = 15.4 \text{ kW}$$

12. Power delivered to both loads (per phase)

$$P_S = (P_L + P_M) / 3 = 5.1 \text{ kW} + 4.3 \text{ kW} = 9.4 \text{ kW}$$