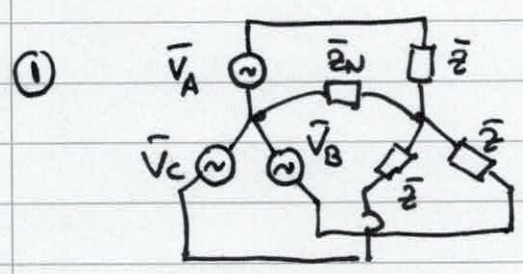


Section A



$$\bar{Y} = 1/\bar{Z} = (0.04 - j0.02) \Omega^{-1}$$


$$\bar{Y}_N = 1/\bar{Z}_N = (-j0.2) \Omega^{-1}$$

$$\bar{V}_N = \frac{\bar{Y}(\bar{V}_A + \bar{V}_B + \bar{V}_C)}{3\bar{Y} + \bar{Y}_N} = (3.3796 - j4.2245) V$$

$$\bar{I}_A = \bar{Y}(\bar{V}_A - \bar{V}_N) = (4.3493 - j1.9634) A$$

$$\bar{I}_B = \bar{Y}(\bar{V}_B - \bar{V}_N) = (-0.2918 + j4.2543) A$$
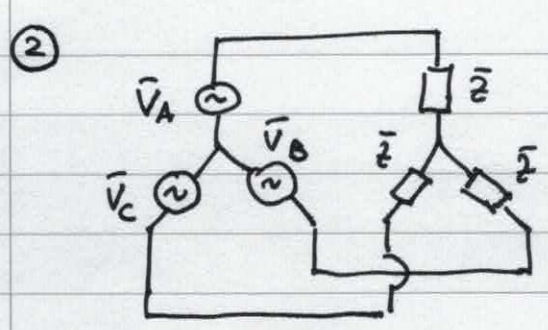
$$\bar{I}_C = \bar{Y}(\bar{V}_C - \bar{V}_N) = (-4.9024 - j2.9668) A$$



In this case $\bar{Y}_N = 0$

Hence:

$$\bar{V}_N = \frac{\bar{Y}(\bar{V}_A + \bar{V}_B + \bar{V}_C)}{3\bar{Y}} = \frac{1}{3}(\bar{V}_A + \bar{V}_B + \bar{V}_C)$$

$$= (0 - j11.547) V$$

Then:

$$\bar{I}_A = \bar{Y}(\bar{V}_A - \bar{V}_N) = (4.6309 - j1.7381) A$$

$$\bar{I}_B = \bar{Y}(\bar{V}_B - \bar{V}_N) = (-0.0102 + j4.4796) A$$

$$\bar{I}_C = \bar{Y}(\bar{V}_C - \bar{V}_N) = (-4.6207 - j2.7414) A$$

Section B

$$\textcircled{3} \quad W = \int i d\lambda = \int k x^3 \lambda^2 d\lambda = \frac{1}{3} k x^3 \lambda^3$$

$$\textcircled{4} \quad W' = \lambda i - W = k x^3 \lambda^3 - \frac{1}{3} k x^3 \lambda^3 = \frac{2}{3} k x^3 \lambda^3$$

where: $\lambda = k^{-1/2} x^{-3/2} i^{1/2}$ (from $i = k x^3 \lambda^2$)

$$\begin{aligned} \text{hence: } W' &= \frac{2}{3} k x^3 k^{-3/2} x^{-9/2} i^{3/2} \\ &= \frac{2}{3} k^{-1/2} x^{-3/2} i^{3/2} \end{aligned}$$

Same result can be obtained from $W' = \int \lambda di = \int k^{-1/2} x^{-3/2} i^{1/2} di$

$$\textcircled{5} \quad f = \left. \frac{\partial W'}{\partial x} \right|_{i \text{ const}} = - \left. \frac{\partial W}{\partial x} \right|_{\lambda \text{ const}}$$

$$\begin{aligned} f &= \left. \frac{\partial W'}{\partial x} \right|_{i \text{ const}} = \frac{2}{3} k^{-1/2} \left(-\frac{3}{2} x^{-5/2} \right) i^{3/2} \\ &= - k^{-1/2} x^{-5/2} i^{3/2} \end{aligned}$$

$$f = - \left. \frac{\partial W}{\partial x} \right|_{\lambda \text{ const}} = - \frac{1}{3} k 3 x^2 \lambda^3 = - k x^2 \lambda^3$$

and, substituting the expression of $\lambda = k^{-1/2} x^{-3/2} i^{1/2}$

$$f = - k x^2 k^{-3/2} x^{-9/2} i^{3/2} = - k^{-1/2} x^{-5/2} i^{3/2} \quad \neq$$

Section C

$$(6) \quad \omega_{s1} = \frac{60 \cdot 60}{4} = 900 \text{ rpm}$$

$$(7) \quad \sigma_N = \frac{\omega_{s1} - \omega_{mN}}{\omega_{s1}} = \frac{900 - 850}{900} = 0.0556 = 5.56\%$$

The electrical power required by the motor is $P_{el} = \frac{P_m}{0.86} = 6081.4 \text{ W}$

Then: $P_{el} = 3 V_N I_L \cos \phi$ where V_N is the phase-to-neutral voltage

$$= 3 \cdot 380 \cdot I_L \cdot 0.7 \quad \Rightarrow \quad I_L = \frac{6081.4}{3 \cdot 380 \cdot 0.7} = 7.621 \text{ A}$$

$$(8) \quad P_{j2} = \sigma_N P_{s1} \quad \text{where} \quad P_{s1} = P_{el} - P_{j1} - P_{Fe}$$

$$P_{s1} = 6081.4 - 410 = 5671.4 \text{ W}$$

$$P_{j2} = 0.0556 P_{s1} = 315 \text{ W}$$

$$\text{Finally} \quad P_{mb} = P_d - P_{j1} - P_{Fe} - P_{j2} - P_m = 126.4 \text{ W}$$

Section D

⑨ in open circuit $E = V$, hence $E_v = 1$

$$\textcircled{10} \quad V = \frac{22000}{\sqrt{3}} = 12701 \text{ V}$$

$$I_N = \frac{S_N}{\sqrt{3} V_N} = \frac{2000000}{\sqrt{3} \cdot 22000} = 52.49 \text{ A}$$

$$\bar{E} = V \angle 0 + (R_a + jX_s) 0.75 I \angle 0 = (13095 + j1968) \text{ V}$$

↑
unity power factor

$$E = |\bar{E}| = 13242 \text{ V}$$

$$E_v = \frac{E - V}{V} = 0.0426 = 4.26 \%$$

$$\textcircled{11} \quad \bar{E} = V \angle 0 + (R_a + jX_s) I (\cos \phi + j \sin \phi) = (11359 + j2315) \text{ V}$$

↑
leading power factor

$$E = |\bar{E}| = 11593 \text{ V}$$

$$E_v = \frac{E - V}{V} = -0.087 = -8.7 \%$$

Section E

$$\textcircled{12} \quad P_1 = 20 \cdot 0.8 = 16 \text{ kW}$$

$$Q_1 = 20 \cdot 0.6 = 12 \text{ KVAr}$$

$$P_2 = 10 \text{ kW}$$

$$Q_2 = -10 \cdot \frac{\sqrt{1-0.7^2}}{0.7} = -10.2 \text{ KVAr}$$

$$P_3 = 10 \text{ kW}$$

$$Q_3 = 0$$

$$P_4 = 8 \frac{0.6}{0.8} = 6 \text{ kW}$$

$$Q_4 = 8 \text{ KVAr}$$

$$P_L = P_1 + P_2 + P_3 + P_4 = 42 \text{ kW}$$

$$Q_L = Q_1 + Q_2 + Q_3 + Q_4 = 9.8 \text{ KVAr} \quad (Q_L > 0)$$

$$\cos \varphi_L = \frac{P_L}{\sqrt{P_L^2 + Q_L^2}} = 0.9738 \quad \text{lagging}$$

$$\textcircled{13} \quad \bar{V}_L = \frac{380}{\sqrt{3}} \angle 0 = 219.4 \angle 0 \text{ V}$$

$$\bar{I}_L = \frac{\bar{S}_L^*}{\bar{V}_L^*} = (0.0638 - j0.0149) \text{ A}$$

$$\bar{V}_S = \bar{V}_L + \bar{Z} \bar{I}_L = (223.65 + j12.46) \text{ V}$$

$$\bar{S}_S = 3 \bar{V}_S \bar{I}_L^* = (42.258 + j12.374) \text{ KVA} = P_S + jQ_S$$

$$\cos \varphi_S = \frac{P_S}{\sqrt{P_S^2 + Q_S^2}} = 0.9597 \quad \text{lagging}$$