

Section A

$$1. \quad \bar{V}_{ab} = (400 \angle 30^\circ) \text{ V} \Rightarrow \begin{aligned} \bar{V}_a &= (230.94 \angle 0^\circ) \text{ V} \\ \bar{V}_b &= (230.94 \angle -120^\circ) \text{ V} \\ \bar{V}_c &= (230.94 \angle +120^\circ) \text{ V} \end{aligned}$$

$$\bar{Z}_A = \bar{Z}_B = \bar{Z}_C = (9 + j12) \Omega$$

$$\begin{aligned} \bar{I}_A &= \frac{\bar{V}_a}{\bar{Z}_A} = Y_A \bar{V}_a = (0.04 - j0.0533)(230.94 \angle 0^\circ) \\ &= (9.2376 - j12.3168) \text{ A} = (15.396 \angle -53.13^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_B &= \bar{I}_A \angle -120^\circ = (-15.2855 - j1.8416) \text{ A} \\ &= (15.396 \angle -173.13^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_C &= \bar{I}_A \angle +120^\circ = (6.048 + j14.158) \text{ A} \\ &= (15.396 \angle 66.87^\circ) \text{ A} \end{aligned}$$

$$\bar{S} = 3 \bar{V}_a \bar{I}_a^* = (6400 + j8533) \text{ VA}$$

$$2. \quad \bar{Y}_A = \frac{1}{\bar{Z}_A} = (0.04 - j0.0533) \Omega^{-1}$$

$$\bar{Y}_B = \frac{1}{\bar{Z}_B} = (0.111 + j0) \Omega^{-1}$$

$$\bar{Y}_C = \frac{1}{\bar{Z}_C} = (0.04 + j0.0533) \Omega^{-1}$$

$$\bar{V}_N = \frac{\bar{Y}_A \bar{V}_a + \bar{Y}_B \bar{V}_b + \bar{Y}_C \bar{V}_c}{\bar{Y}_A + \bar{Y}_B + \bar{Y}_C} = (-98.78 - j171.09) \text{ V}$$

$$\begin{aligned} \bar{I}_A &= \bar{Y}_A (\bar{V}_a - \bar{V}_N) = (22.314 - j10.741) \text{ A} \\ &= (24.764 \angle -25.7^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_B &= \bar{Y}_B (\bar{V}_b - \bar{V}_N) = (-1.855 - j3.212) \text{ A} \\ &= (3.709 \angle -119.9^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_C &= \bar{Y}_C (\bar{V}_c - \bar{V}_N) = \cancel{(20.46 + j13.953) \text{ A}} \\ &= (-20.46 + j13.953) \text{ A} \\ &= (24.764 \angle 145.7^\circ) \text{ A} \end{aligned}$$

$$\bar{S} = \bar{V}_a \bar{I}_A^* + \bar{V}_b \bar{I}_B^* + \bar{V}_c \bar{I}_C^* = (11162.8 + j0) \text{ VA}$$

#

Section B

$$3. \begin{cases} i_1(t) = 10 \sin(200t) \\ i_2(t) = 0 \end{cases}$$

$$e_2 = \frac{d\lambda_2}{dt} = \frac{d}{dt} (L_{21} i_1 + L_{22} i_2) = \\ = \frac{d}{dt} [(0.05 \cos \theta) (10 \sin 200t)]$$

$$\text{since } \theta = \omega t + \delta = 200t + \delta$$

then

$$e_2 = \frac{d}{dt} [(0.05 \cos(200t + \delta)) (10 \sin 200t)] = 100 \cos(200t + \delta)$$

where δ is an angular position that depends on the initial position of the rotor w.r.t. the angular reference of the current i_1 .

4. The expression of the mechanical torque is:

$$T = \frac{1}{2} i_1^2 \frac{dL_{11}}{d\theta} + \frac{1}{2} i_2^2 \frac{dL_{22}}{d\theta} + i_1 i_2 \frac{dL_{12}}{d\theta} \\ = (-0.05 \sin \theta) i_1 i_2$$

$$\text{since } i_1 = i_2 = 10 \sin 200t \quad \text{and} \quad \theta = \omega t + \delta$$

$$\text{one obtains: } T = -0.05 \sin(\omega t + \delta) 100 \sin^2(200t) = \\ = -2.5 \sin(\omega t + \delta) + 2.5 \cos(400t) \sin(\omega t + \delta)$$

→ the average T is not null, thus, is $\omega = 400 \text{ rad/s}$


#

Section C

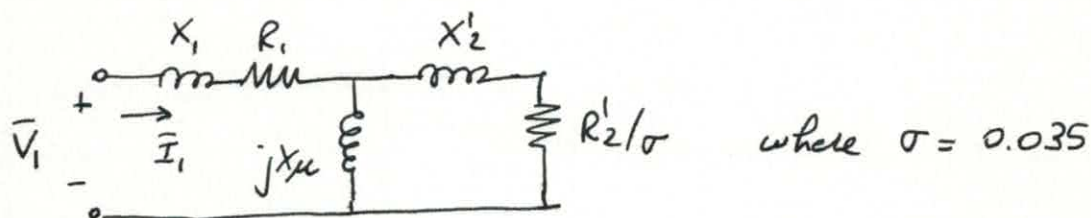5. Let us first refer the rotor parameters to the stator:

$$R_2' = k_T^2 R_2 = 4^2 \cdot 0.025 = 0.4 \Omega$$

$$X_2' = k_T^2 X_2 = 4^2 \cdot 0.05 = 0.8 \Omega$$



$$\bar{I}_1 = \bar{V}_1 / \bar{Z}_{eq} \quad \text{where } \bar{V}_1 = \left(\frac{230}{\sqrt{3}} \angle 0 \right) V$$

$$= (10.720 - j3.747) A$$

$$\bar{Z}_{eq} = \bar{Z}_1 + \frac{\bar{Z}_2'(\sigma) \bar{Z}_\mu}{\bar{Z}_2' + \bar{Z}_\mu} = (11.038 + j3.858) \Omega$$

$$\text{with } \bar{Z}_1 = R_1 + jX_1 = (0.5 + j0.7) \Omega$$

$$\bar{Z}_2' = R_2'/\sigma + jX_2' = (11.43 + j0.8) \Omega$$

$$\bar{Z}_\mu = 0 + jX_\mu = (50j) \Omega$$

$$\bar{S}_1 = 3 \bar{V}_1 \cdot \bar{I}_1^* = (4270.7 + j1492.8) VA$$

$$\cos \varphi_1 = 0.946 \quad (\text{lagging})$$

$$6. \quad \sigma_M = \frac{R_2'}{\sqrt{R_1^2 + (X_1 + X_2')^2}} = 0.253 \Rightarrow I_{1M} = (52.172) A$$

$$T_{max} = \frac{3P}{\omega_1} I_{1M}^2 \frac{R_2'}{\sigma_M} = 123.3 \text{ Nm}$$

where $p=3$, $\omega_1 = 2\pi \cdot 50 = 314.16 \text{ rad/s}$ and I_{1M} is calculated as I_1 above but for $\sigma = \sigma_M$.

At startup, $\sigma = 1$, hence:

$$I_{\text{start}} = \frac{\bar{V}_i}{\bar{z}_{\text{eq}}(\sigma=1)} = 76.55 \text{ A}$$

✘

Section D

7. Phase voltage at the stator of the generator:

$$\bar{V} = \frac{1100}{\sqrt{3}} = (6350.85 \angle 0^\circ) \text{ V}$$

The internal emf is given by:

$$\begin{aligned} \bar{E} &= \bar{V} + jX_s \bar{I} = 6350.85 \angle 0^\circ + j10 \cdot 220 \angle 0^\circ \\ &= (6721.11 \angle 19.11^\circ) \text{ V} \end{aligned}$$

The increased emf is $E' = 1.25 \cdot 6721.11 = 8401.39 \text{ V}$

The initial mechanical power is:

$$P_m = P_e = \sqrt{3} \cdot 1100 \cdot 220 = 4191563 \text{ W}$$

Since P_m is assumed to remain unchanged:

$$P_m = \frac{3 E' V}{X_s} \sin \delta \Rightarrow \sin \delta = 0.2618 \Rightarrow \delta = 15.18^\circ$$

hence $\bar{E}' = E' \angle \delta$. Then, one has:

$$\bar{E}'_0 = \bar{V} + jX_s \bar{I}'_s \Rightarrow 8401.4 \angle 15.18^\circ = 6350.85 \angle 0^\circ + \bar{I}'_s \cdot j10$$

$$\Rightarrow \bar{I}'_s = (281.5 \angle 38.61^\circ) \text{ A}$$

$$I'_s = 281.5 \text{ A}$$

$$\varphi_s = 38.61^\circ$$

8. The maximum power is obtained for a load angle of 90° .

Hence:

$$P_{\max} = 3 \frac{E'V}{X_s} \sin 90^\circ = 3 \frac{8401.39 \cdot 6350.85}{10} = 16 \text{ MW}$$

Then:

$$\bar{E}'_q = \bar{V} + jX_s \bar{I}_{S\max} \Rightarrow 8401.39 \angle 90^\circ = 6350.85 \angle 0^\circ + j10 \bar{I}_{S\max}$$

$$\Rightarrow \bar{I}_{S\max} = (1053.17 \angle 37.09^\circ) \text{ A}$$

$$I_{S\max} = 1053.17 \text{ A}$$

$$\varphi_{S\max} = 37.09^\circ$$

///

Section E

9. Let us calculate first the complex power for each load:

$$\begin{cases} \bar{S}_1 = 700 \angle 36.9^\circ = (560 + j420) \text{ kVA} \\ \bar{S}_2 = 1000 \angle 60^\circ = (500 + j866) \text{ kVA} \\ \bar{S}_3 = 800 \angle 25.8^\circ = (720 + j349) \text{ kVA} \end{cases}$$

The total complex power is:

$$\begin{aligned} \bar{S}_T &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = (1780 + j1635) \text{ kVA} \\ &= (2417 \angle 42.57^\circ) \text{ kVA} \end{aligned}$$

We also have that $|\bar{S}_T| = \sqrt{3} V_S I_S$

hence:
$$I_S = \frac{2417 \cdot 10^3}{\sqrt{3} \cdot 13.8 \cdot 10^3} = 101.1 \text{ A}$$

The combined power factor is:

$$\cos \varphi_S = \frac{1780}{2417} = 0.7365 \text{ (lagging)}$$

10. a power factor equal to 0.92 lagging corresponds to $\cos \varphi = 0.92 \Rightarrow \varphi = 23.07^\circ$.

Therefore the new complex power at the source is:

$$\begin{aligned}\bar{S}_{T_{\text{new}}} &= 1780 + j 1780 \tan(23.07^\circ) \\ &= (1780 + j 758.28) \text{ kVA}\end{aligned}$$

$$\bar{S}_{\text{cap}} = \bar{S}_{T_{\text{new}}} - \bar{S}_T = j Q_C$$

$$\Rightarrow j Q_C = j(758.28 - 1635) = (-j 876.72) \text{ kVA}$$

$$-j \omega C V_s^2 = -j \frac{876.72 \cdot 10^3}{3}$$

Assuming a frequency of 50 Hz and $V_s = 13.8 \text{ kV}$ (line-to-line)

then $\omega = 2\pi \cdot 50 = 314.16 \text{ rad/s}$

$$\Rightarrow C = 4.885 \mu\text{F}$$

///