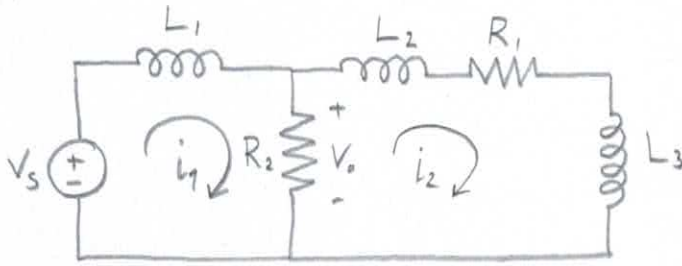


MIDTERM EXAMINATION

EEEN20090 - ELECTRICAL ENERGY SYSTEMS

SECTION A



$$\begin{aligned} L_1 &= 8 \text{ H} & R_1 &= 50 \Omega \\ L_2 &= 6 \text{ H} & R_2 &= 400 \Omega \\ L_3 &= 3 \text{ H} \end{aligned}$$

$$V_s(t) = 25 \cos(40t + 45^\circ) \text{ V}$$

1. $i_1(t)$ & $i_2(t)$?

$$\bar{V}_s = \frac{25}{\sqrt{2}} \angle 45^\circ \text{ RMS} \quad \text{and } \omega = 40$$

and

$$X_1 = \omega L_1 = 40 \cdot 8 = 320 \Omega$$

$$X_2 = \omega L_2 = 40 \cdot 6 = 240 \Omega$$

$$X_3 = \omega L_3 = 40 \cdot 3 = 120 \Omega$$

$$\begin{aligned} \bar{I}_1 &= \frac{\bar{V}_s}{\bar{Z}_{\text{total}}} \quad \text{where } \bar{Z}_{\text{total}} = jX_1 + R_2 \parallel (R_1 + j(X_2 + X_3)) \\ &= \frac{25}{\sqrt{2}} \angle 45^\circ \\ &= \frac{526,11 \angle 69,7^\circ}{526,11 \angle 69,7^\circ} \\ &= 33,6 \angle -24,7^\circ \text{ mA} \end{aligned}$$

$$\begin{aligned} \bar{Z}_{\text{total}} &= jX_1 + \frac{R_2(R_1 + j(X_2 + X_3))}{R_2 + (R_1 + j(X_2 + X_3))} \\ &= j320 + \frac{400(50 + j(240 + 120))}{400 + 50 + j(240 + 120)} \\ &= 526,11 \angle 69,7^\circ \Omega \end{aligned}$$

$$\begin{aligned} i_1(t) &= 33,6 \cdot \sqrt{2} \cos(40t - 24,7^\circ) \\ &= \underline{\underline{47,5 \cos(40t - 24,7^\circ) \text{ mA}}} \end{aligned}$$

$$\bar{I}_2 = \bar{I}_1 \cdot \frac{R_2}{R_1 + R_2 + j(X_2 + X_3)} = 23,32 \angle -63,35^\circ \text{ mA}$$


$$i_2(t) = \underline{\underline{32,98 \cos(40t - 63,35^\circ) \text{ mA}}}$$

SECTION A

② $V_o(t)$?

$$\begin{aligned}\bar{V}_o &= \bar{V}_s - \bar{I}_1 \cdot X_1 = \frac{25}{\sqrt{2}} \angle 45^\circ - 33,6 \cdot 10^{-3} \angle -24,7^\circ \cdot 320 \angle 90^\circ \\ &= 8,461 \angle 18,8^\circ\end{aligned}$$
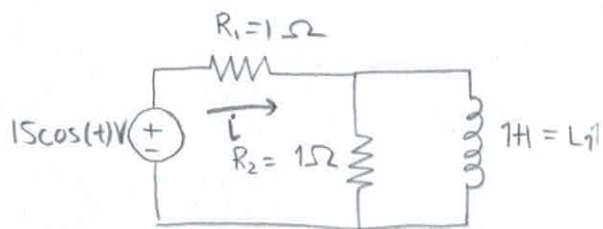
$$\begin{aligned}V_o(t) &= \sqrt{2} \cdot 8,461 \cos(40t + 18,8^\circ) \\ &= \underline{\underline{11,97 \cos(40t + 18,8^\circ)}}\end{aligned}$$



$$\omega = 1 \Rightarrow X_1 = \omega L_1 = 1 \Omega$$

$$\bar{V} = \frac{15}{\sqrt{2}} \angle 0^\circ$$

③ The average power delivered by the source to the circuit?

First find current from source

$$\bar{I} = \frac{\bar{V}}{\bar{Z}_{eq}} \quad \text{where } \bar{Z}_{eq} = R_1 + R_2 \parallel jX_1 = 1 + \frac{1 \cdot j1}{1 + j1} = \frac{\sqrt{10}}{2} \angle 18,4^\circ$$

$$\Rightarrow \bar{I} = \frac{\frac{15}{\sqrt{2}} \angle 0^\circ}{\frac{\sqrt{10}}{2} \angle 18,4^\circ} = 3\sqrt{5} \angle -18,4^\circ$$

changes sign of angle

$$\text{Find } \bar{S} = \bar{V} \cdot \bar{I}^* = \frac{15}{\sqrt{2}} \angle 0^\circ \cdot 3\sqrt{5} \angle 18,4^\circ = 71,15 \angle 18,4^\circ \text{ VA}$$

The active power delivered:


$$P = \text{Re}\{\bar{S}\} = 71,15 \cos(18,4^\circ) = \underline{\underline{67,5 \text{ W}}}$$

④ The power absorbed by the resistor R_1 .

$$P_1 = R_1 I^2 = \underline{\underline{45 \text{ W}}}$$

SECTION B

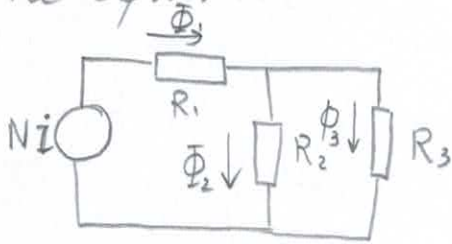The equivalent circuit for the magnetic system:



where

$$l_1 = l_3 = 300 \text{ mm}$$

$$l_2 = 100 \text{ mm}$$

$$A_1 = A_3 = 200 \text{ mm}^2$$

$$A_2 = 400 \text{ mm}^2$$

$$\mu_{r1} = \mu_{r3} = 2250$$

$$N = 25$$

5. Φ_1, Φ_2 & Φ_3 ?
for $i = 0.5 \text{ A}$

Find reluctances:

$$R_1 = R_3 = \frac{l_1}{\mu_r \mu_0 A_1} = \frac{300 \cdot 10^{-3}}{2250 \cdot 4\pi \cdot 10^{-7} \cdot 200 \cdot 10^{-6}} = 0.531 \cdot 10^6 \text{ A/Wb}$$

$$R_2 = \frac{100 \cdot 10^{-3}}{1350 \cdot 4\pi \cdot 10^{-7} \cdot 400 \cdot 10^{-6}} = 0.148 \cdot 10^6 \text{ A/Wb}$$

$$R_t = R_1 + R_2 \parallel R_3 = 0.6458 \cdot 10^6 \text{ A/Wb}$$

$$\Phi_1 = \frac{N \cdot i}{R_t} = \underline{\underline{19.36 \cdot 10^{-6} \text{ Wb}}}$$

$$\Phi_2 = \frac{R_3}{R_2 + R_3} \Phi_1 = \underline{\underline{15.15 \cdot 10^{-6} \text{ Wb}}}$$

$$\Phi_3 = \Phi_1 - \Phi_2 = \underline{\underline{4.21 \cdot 10^{-6} \text{ Wb}}}$$

6. B_1, B_2 & B_3 ? for $i = 0.5 \text{ A}$

$$B_1 = \Phi_1 / A_1 = 19.36 \cdot 10^{-6} / 200 \cdot 10^{-6} = \underline{\underline{0.0968 \text{ T}}}$$

$$B_2 = \Phi_2 / A_2 = 15.15 \cdot 10^{-6} / 400 \cdot 10^{-6} = \underline{\underline{0.03788 \text{ T}}}$$


$$B_3 = \Phi_3 / A_3 = 4.21 \cdot 10^{-6} / 200 \cdot 10^{-6} = \underline{\underline{0.02105 \text{ T}}}$$

SECTION B

7. Self-inductance of the magnetic circuit?

$$L = \frac{N\Phi_1}{i} = \frac{25 \cdot 19,36 \cdot 10^{-6}}{0,5} = \underline{\underline{0,000968 \text{ H}}}$$

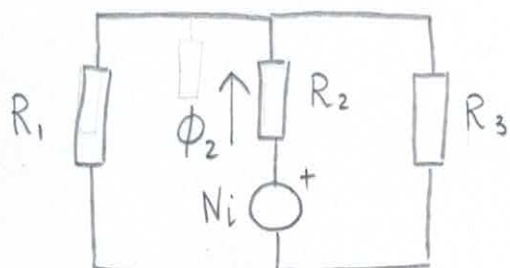8. The self-inductance of the magnetic circuit if the coil is moved to the central part of the magnetic circuit.



$$\begin{aligned} R_{\text{total}} &= R_2 + R_3 \parallel R_1 \\ &= R_2 + \frac{R_3 R_1}{R_3 + R_1} = 0,413 \cdot 10^6 \text{ A/Wb} \end{aligned}$$

$$\Phi_2 = \frac{Ni}{R_{\text{total}}} = \frac{25 \cdot 0,5}{0,413 \cdot 10^6} = 30,3 \cdot 10^{-6} \text{ Wb}$$

$$L = \frac{N \cdot \Phi_2}{i} = \frac{25 \cdot 30,3 \cdot 10^{-6}}{0,5} = \underline{\underline{0,001515 \text{ H}}}$$

SECTION C

Nominal parameters of transformer:

$$S_N = 200 \text{ kVA}, V_{1N} = 13,200 \text{ V}, V_{2N} = 2,200 \text{ V}$$

Open-circuit test: 2,200 V, 3,1 A & 1,550 W

Short-circuit test: 210 V, 90,9 A & 2,500 W

Transformer is feeding a load consuming:

$$S_2 = 180 \text{ kVA}, \text{ Pf } \cos(\phi_2) = 0,9 \text{ leading}, V_2 = V_{2N}$$

9. G_{Fe}'' & B_{μ}'' ?

Use the results from the open circuit test:


$$R_{Fe}'' = \frac{V''^2}{P''} = \frac{2,200^2}{1,550} = 3,123 \Omega$$

$$\Rightarrow G_{Fe}'' = \frac{1}{R_{Fe}''} = \underline{\underline{0,00032}}$$

$$I_{Fe}'' = \frac{2,200}{R_{Fe}''} = 0,7045 \text{ A}$$

$$I_{\mu}'' = \sqrt{3,1^2 - 0,7045^2} = 3,0189 \text{ A}$$
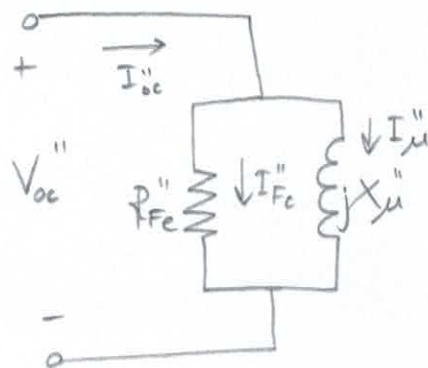
$$X_{\mu}'' = \frac{2,200}{3,0189} = 728,7 \Omega \Rightarrow B_{\mu}'' = \frac{1}{X_{\mu}''} = \underline{\underline{0,001372}}$$



10. R_{sc}'' & X_{sc}'' ?


Use the short circuit test results:

$$R_{sc}'' = \frac{P_{sc}}{I_{sc}^2} = \frac{2,500}{90,9^2} = \underline{\underline{0,3026 \Omega}}$$

$$Z_{sc}'' = \frac{210}{90,9} = 2,31 \Omega$$

$$X_{sc}'' = \sqrt{Z_{sc}''^2 - R_{sc}''^2}$$
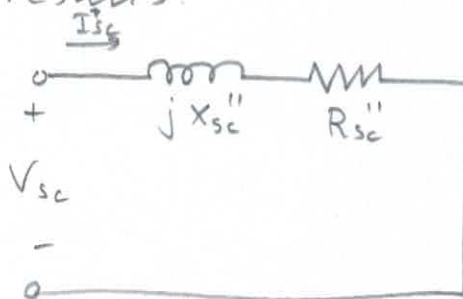
$$= \sqrt{2,31^2 - 0,3026^2} = \underline{\underline{2,29 \Omega}}$$




SECTION C

11. The voltage regulation at the given operating condition?

$$E_v = 100 \frac{|V_1'' - V_2|}{|V_1''|} \quad \leftarrow \text{known}$$

Need to find V_1'' . Circuit model:

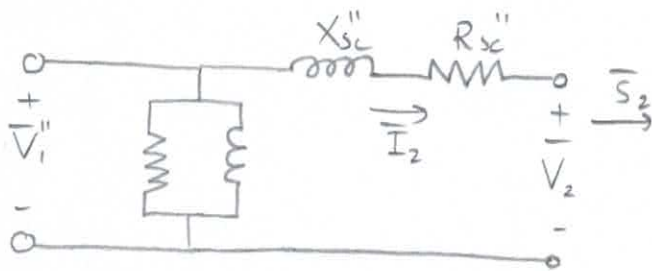

$$\cos(\varphi_2) = 0,9 \Rightarrow \varphi_2 = -25,84^\circ$$

leading ↑ negative because is leading

$$\Rightarrow \sin(\varphi_2) = -0,436$$

$$\text{Then we have: } |\bar{I}_2| = \frac{|S_2|}{|V_2|} = \frac{180 \cdot 10^3}{2200} = 81,82 \text{ A}$$

$$\text{and: } V_2 = V_1'' - I_2(R_{sc}'' \cos(\varphi_2) + X_{sc}'' \sin(\varphi_2))$$

$$\Rightarrow V_1'' = V_2 + I_2(R_{sc}'' \cos(\varphi_2) + X_{sc}'' \sin(\varphi_2))$$

$$= 2140,6 \text{ V}$$

and calculate:

$$E_v = 100 \frac{|V_1'' - V_2|}{|V_1''|} = \underline{\underline{27,75}}$$

12. Efficiency?

$$\eta = \frac{P_2}{P_2 + P_{Fe} + P_{\mu}}$$

$$P_{Fe} = V_1''^2 G_{Fe} = 2140,6^2 \cdot 0,00032 = 1,46 \text{ kW}$$

$$P_{\mu} = R_{sc}'' \cdot I_2^2 = 0,3026 \cdot 81,82^2 = 2,026 \text{ kW}$$

$$P_2 = S_2 \cos(\varphi) = 180 \cdot 0,9 = 162 \text{ kW}$$

$$\eta = \frac{162}{162 + 1,46 + 2,026} = 0,979 \approx \underline{\underline{98\%}}$$