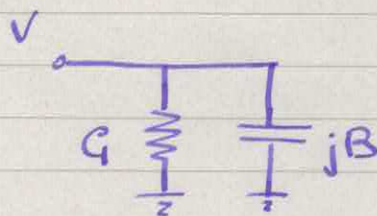


EEN20090

Section A

1. Equivalent circuit:



$$V = 20 \text{ kV}$$

$$Q = 200 \text{ kVar}$$

$$P = 2 \text{ kW}$$

 $B > 0 \rightarrow$  capacitor

$$\bar{Y} = G + jB$$

$$B = \frac{Q}{V^2} = \frac{200 \cdot 10^3}{(20 \cdot 10^3)^2} = 5 \cdot 10^{-4} \Omega^{-1}$$

$$G = \frac{P}{V^2} = \frac{2 \cdot 10^3}{(20 \cdot 10^3)^2} = 5 \cdot 10^{-6} \Omega^{-1}$$

$$2. \quad \bar{Z} = \frac{1}{\bar{Y}} = R + jX$$

$$R = 20 \Omega, \quad X = -2000 \Omega \rightarrow \text{capacitive element.}$$


In both cases, the element has to be implemented as a capacitor. The conductance can be assumed to be due to the losses of the capacitor - No additional element is thus required.



EEEN20090

## Section B.

3. Equivalent magnetic circuit

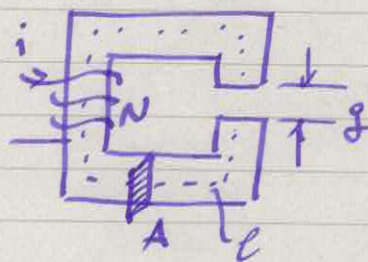

$$A = 20 \cdot 10^{-4} \text{ m}^2$$

$$l = 0.1 \text{ m}$$

$$g = 2 \cdot 10^{-3} \text{ m}$$

$$B = \frac{2H}{230 + H} \Rightarrow H = \frac{230 B}{2 - B} \quad \text{in the iron core}$$

Equations:  $\phi = \phi_g$  (no fringing effect)

$$BA = B_g A \rightarrow B = B_g$$

$$B_g = \mu_0 H_g = B \Rightarrow H_g = B / \mu_0$$

and, finally, from the Ampere's law:  $Ni = Hl + H_g g$

Substituting and solving for B:

$$\frac{230 B}{2 - B} l + \frac{B}{\mu_0} g = Ni$$





EEEN 20090

$$\rightarrow (230 \ell + Ni + 2g/\mu_0) B - \frac{g}{\mu_0} \cdot B^2 - 2Ni = 0$$

$$\rightarrow a B^2 + b B + c = 0$$

where:  $a = \frac{g}{\mu_0} = 1591.55$

$$b = - \left( 230 \cdot \ell + Ni + \frac{2g}{\mu_0} \right) = -4206.1$$

$$c = 2Ni = 2000$$

hence  $B = \begin{cases} 2.021 \text{ T} \\ 0.622 \text{ T} \end{cases} \rightarrow \text{only acceptable solution (because positive H)}$

$$H = \frac{230 B}{2 - B} = 103.82 \text{ A-t}$$

$$\phi = B \cdot A = 0.622 \cdot 2 \cdot 10^{-4} = 0.00124 \text{ Wb}$$

$$4. \quad \mu = \frac{B}{H} = \frac{0.622}{103.82} = 0.006 \text{ [H/m]}$$

$$\mu_r = \frac{\mu}{\mu_0} = 4768 \approx 5000 \rightarrow \text{typical iron alloy for magnetic circuits}$$



EEEN 20090

$$5. \quad L = \frac{N^2}{R_{TOT}}$$

$$\text{where } R_{TOT} = R_{Fe} + R_g$$

$$R_{Fe} = \frac{l}{\mu A} = \frac{0.1}{20 \cdot 10^{-4} \cdot 2006} = 8333 \text{ H}^{-1}$$

$$R_g = \frac{l}{\mu_0 A} = \frac{2 \cdot 10^{-3}}{20 \cdot 10^{-4} \cdot 4 \cdot \pi \cdot 10^{-7}} = 795775 \text{ H}^{-1}$$

$$R_{TOT} = 804108 \text{ H}^{-1}$$

$$L = \frac{500^2}{R_{TOT}} = 0.311 \text{ [H]} \quad \#$$



EEEN 20090

## Section C

$$6. \quad K_T = \frac{2400}{240} = 10$$

$$\left\{ \begin{array}{l} R_1'' = 3/10^2 = 0.03 \, \Omega \\ X_1'' = 15/10^2 = 0.15 \, \Omega \end{array} \right.$$

$$\left\{ \begin{array}{l} R_{sc}'' = R_1'' + R_2 = 0.06 \, \Omega \\ X_{sc}'' = X_1'' + X_2 = 0.3 \, \Omega \end{array} \right.$$

$$\bar{z}_{sc}'' = R_{sc}'' + jX_{sc}''$$

$$I_{2N} = \frac{S_N}{V_{2N}} = \frac{10000}{240} = 41.7 \, A$$

$$\bar{V}_2 = V_2 \angle 0 \rightarrow \text{phase reference} \rightarrow \bar{I}_2 = 41.7 \angle -36.87^\circ$$

$$\cos \phi_2 = 0.8$$

$$\rightarrow \bar{V}_1'' = \bar{V}_2 + \bar{I}_2 \cdot \bar{z}_{sc}'' = 250.65 \angle 1.952^\circ \, V$$

lagging

$$V_1 = V_1'' \cdot K_T = 2496.5 \, V$$

$$E_V = \frac{250.65 - 240}{250.65} \cdot 100 = 4.25 \%$$





EEEN20090

$$7. \quad \bar{I}_2 = 41.7 \angle 36.87^\circ \text{ A}$$

$$\uparrow \cos \phi = 0.8 \text{ lagging}$$

$$\bar{V}_1'' = \bar{V}_2 + \bar{I}_2 \bar{Z}_{sc}'' = 234.78 \angle 2.81^\circ \text{ V}$$

$$V_1 = k_T V_1'' = 2,347.8 \text{ V}$$

$$e_V = \frac{234.78 - 240}{234.78} \cdot 100 = -2.22 \%$$

