

Section A

$$1. \quad \bar{V} = \bar{z}_2 \cdot \bar{I} \quad \text{where} \quad \bar{I} = \frac{\bar{V}_3}{\bar{z}_1 + \bar{z}_2}$$


$$\bar{V}_3 = \frac{15}{\sqrt{2}} \angle 0 = (10.607 \angle 0) \text{ V}$$

$$\bar{I} = \frac{10.607 \angle 0}{(13.97 - j6.247) + (8.646 + j11.515)} = (0.445 - j0.104) \text{ A}$$

$$\begin{aligned} \bar{V} &= (8.646 + j11.515)(0.445 - j0.104) = (5.04 + j4.227) \text{ V} \\ &= (6.578 \angle 0.698) \text{ V} = (6.578 \angle 39.986^\circ) \text{ V} \end{aligned}$$

$$v(t) = \sqrt{2} \cdot 6.578 \cos(20t + 0.698) \text{ V} = 9.303 \cos(20t + 0.698) \text{ V}$$

2. \bar{z}_1 , series connection

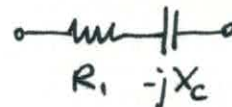

$$\bar{z}_1 = z_1 \angle \varphi_1$$

$$R_1 = z_1 \cos \varphi_1$$


$$X_c = z_1 |\sin \varphi_1|$$

$$R_1 = 13.966 \Omega$$

$$X_c = 6.247 \Omega$$

$$X_c = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_c} = \frac{1}{20 \cdot 6.247} = 0.008 \text{ F}$$

\bar{z}_2 , parallel connection

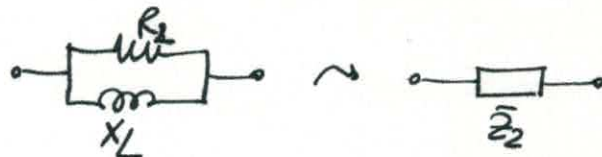

$$\rightarrow \bar{Y}_2 = \frac{1}{\bar{z}_2} = (0.0417 - j0.0555) \Omega^{-1} = G_2 - jB_2$$

$$R_2 = \frac{1}{G_2} = 4973 \Omega$$

$$X_L = \frac{1}{B_2} = 3733 \Omega$$

$$X_L = \omega L \Rightarrow L = \frac{X_L}{\omega} = 186.7 \text{ H}$$


$$3. \quad P_{R1} = R_1 \cdot I^2 = R_1 \cdot |\bar{I}|^2 = 2.915 \text{ W}$$

$$P_{R2} = G_2 \cdot V^2 = G_2 \cdot |\bar{V}|^2 = 1.804 \text{ W}$$

$$\bar{S}_g = \bar{V}_g \cdot \bar{I}^* = (4.719 + j1.099) \text{ VA}$$

Section B

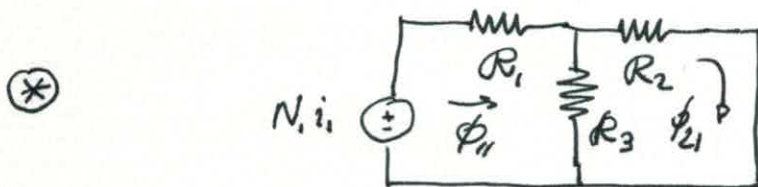
4. $L_{11} = N_1 \frac{\phi_{11}}{i_1}$ where ϕ_{11} is determined by the following circuit:



and, hence, one has:
$$\phi_{11} = \frac{R_2 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} N_1 i_1$$

Then:
$$L_{11} = N_1^2 \frac{R_2 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

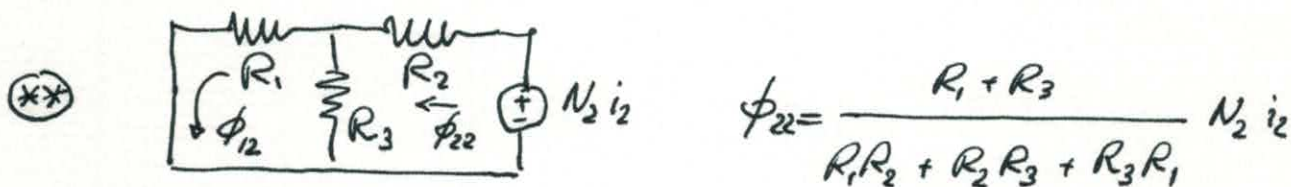Equivalently $L_{22} = N_2 \frac{\phi_{22}}{i_2}$ where ϕ_{22} is given by:



and, hence, one has:
$$L_{22} = N_2^2 \frac{R_1 + R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

5. $L_{21} = N_2 \frac{\phi_{21}}{i_1}$ where ϕ_{21} is determined from circuit (*) as:

$$\phi_{21} = \phi_{11} \frac{R_3}{R_2 + R_3}$$

then:
$$L_{21} = N_1 N_2 \frac{R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

Equivalently, one can determine $L_{12} = N_1 \frac{\phi_{12}}{i_2}$ where, from circuit (**), one has:

$$\phi_{12} = \phi_{22} \frac{R_3}{R_1 + R_3}$$

and, finally:

$$L_{12} = N_1 N_2 \frac{R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

6. From the solution of 4. and 5., we observe that

$$M = L_{12} = L_{21} \neq \sqrt{L_{11} L_{22}}$$

This result is as expected because:

a. No flux leakage is assumed

b. $\phi_{11} \neq \phi_{21}$ and $\phi_{22} \neq \phi_{12}$

The condition $M = \sqrt{L_{11} L_{22}}$ holds only in circuits for which the flux in both windings is the same.

One can define a "coupling coefficient" as follows:

$$\left. \begin{aligned} K_1 &= \frac{\phi_{21}}{\phi_{11}} = \frac{R_3}{R_2 + R_3} \\ K_2 &= \frac{\phi_{12}}{\phi_{22}} = \frac{R_3}{R_1 + R_3} \end{aligned} \right\} \Rightarrow M = K \sqrt{L_{11} L_{22}}$$

$$K = \sqrt{K_1 K_2} = \frac{R_3}{\sqrt{(R_2 + R_3)(R_1 + R_3)}}$$

hence $M = \sqrt{L_{11} L_{22}}$ only if the coupling coefficient $K = 1$ #

Section C

$$7. \quad V_1 = 2000 \text{ V}, \quad I_{10} = 1 \text{ A}, \quad P_0 = 1000 \text{ W}$$

$$P_0 = V_1 I_{10} \cos \varphi_0 \Rightarrow \cos \varphi_0 = 0.5$$

$$\sin \varphi_0 = 0.866$$

$$\Rightarrow I_{Fe} = I_{10} \cos \varphi_0 = 0.5 \text{ A}$$

$$I_{\mu} = I_{10} \sin \varphi_0 = 0.866 \text{ A}$$

$$\Rightarrow R_{Fe} = \frac{V_1}{I_{Fe}} = \frac{2000}{0.5} = 4000 \Omega$$

$$X_{\mu} = \frac{V_1}{I_{\mu}} = \frac{2000}{0.866} = 2309.5 \Omega$$

$$8. \quad V_{isc} = K_T V_{2sc} = \frac{2000}{200} \cdot 8 = 80 \text{ V}$$

$$I_{isc} = I_{IN} = \frac{S_N}{V_{IN}} = \frac{160000}{2000} = 80 \text{ A}$$

$$P_{sc} = 2560 \text{ W}$$

$$P_{sc} = V_{isc} \cdot I_{IN} \cos \varphi_{sc} \Rightarrow \cos \varphi_{sc} = 0.4$$

$$\sin \varphi_{sc} = 0.917$$

$$Z'_{sc} = \frac{V_{isc}}{I_{IN}} = 1 \Omega \Rightarrow R'_{sc} = Z'_{sc} \cdot \cos \varphi_{sc} = 0.4 \Omega$$

$$X'_{sc} = Z'_{sc} \cdot \sin \varphi_{sc} = 0.917 \Omega$$

9. From Kapp's formula, one has:

$$V_1 = V_2' + R'_{sc} I_2' \cos \varphi_2 + X'_{sc} I_2' \sin \varphi_2$$

where:

$$V_1 = 2000 \text{ V}$$

$$I_2 = 400 \text{ A} \Rightarrow I_2' = \frac{400}{k_T} = \frac{400}{10} = 40 \text{ A}$$

$$\cos \phi_2 = 0.8 \text{ (lagging)} \Rightarrow \sin \phi_2 = 0.6$$

hence:

$$2000 = V_2' + 0.4 \cdot 40 \cdot 0.8 + 0.917 \cdot 40 \cdot 0.6$$

$$\Rightarrow V_2' = 1965.2 \text{ V} \Rightarrow V_2 = \frac{V_2'}{k_T} = 196.52 \text{ V}$$

10. The efficiency is maximum when the losses in the iron are equal to the losses in the windings. This is equivalent to impose a power consumption equal to:

$$S_{\eta \max} = \sqrt{\frac{P_0}{P_{sc}}} \cdot S_N = \sqrt{\frac{1000}{2560}} \cdot 160 = 100 \text{ KVA}$$

Then, the maximum efficiency is given by:

$$\eta_{\max} = \frac{S_{\eta \max} \cos \phi}{S_{\eta \max} \cos \phi + 2P_0} = \frac{100 \cdot 0.8}{100 \cdot 0.8 + 2 \cdot 1} = \frac{80}{82} = 97.56\%$$

#