

1st term, year 2018/19SECTION A

The equations of the two meshes shown in Fig 1 are:

$$(10 + j0) \bar{I}_1 + (10 + j10) \bar{I}_1 - (10 + j0) \bar{I}_2 = 212 \angle 90^\circ$$

$$-(10 + j10) \bar{I}_1 + (10 + j10) \bar{I}_2 + (0 - j20) \bar{I}_2 = 212 \angle -150^\circ$$

Substituting and solving for each current, gives:

$$\bar{I}_1 = 3.66 \angle 15^\circ \text{ A}$$

$$\bar{I}_2 = 11.96 \angle -113.8^\circ \text{ A}$$

From the circuit, one has:

$$\bar{I}_{a'a} = \bar{I}_1$$

$$\bar{I}_{c'c} = -\bar{I}_2 = 11.96 \angle 66^\circ \text{ A}$$

$$\bar{I}_{b'b} = -\bar{I}_{a'a} + \bar{I}_{c'c} = -\bar{I}_1 + \bar{I}_2 = 14.54 \angle -125.1^\circ \text{ A}$$

✱

① The stored energy is:

$$W = W' = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

Substituting the expressions of L_1 , L_2 and M , and the values of i_1 and i_2 , one has:

$$W = \frac{1}{2} (5 + 2 \cos 2\theta) i_1^2 + \frac{1}{2} (3 + \cos 2\theta) 0.5^2 + 10 \cos \theta \cdot 1 \cdot 0.5$$

$$= 2.5 + \cos 2\theta + 0.375 + 0.125 \cos 2\theta + 5 \cos \theta$$

$$= 2.875 + 1.125 \cos 2\theta + 5 \cos \theta$$

② The mechanical torque is:

$$T = \left. \frac{\partial W'}{\partial \theta} \right|_{i = \text{const.}} = -2.25 \sin 2\theta - 5 \sin \theta$$

#

SECTION C

3. Synchronous speed : $n_1 = \frac{60 \cdot 50}{2} = 1500 \text{ rpm}$

Nominal speed : $n = n_1 (1 - s_N) = 1500(1 - 0.04) = 1440 \text{ rpm}$

4. Start-up current: $I_{\text{sup}} = \left| \frac{380/\sqrt{3} \angle 0}{(0.1 + j0.4) + (0.1 + j0.3)} \right| = 301.4 \text{ A}$

Nominal current: $I'_{2N} = I_{1N} = \frac{380/\sqrt{3} \angle 0}{\left| (0.1 + j0.4) + \left(\frac{0.1}{0.04} + j0.3 \right) \right|} = 81.48 \text{ A}$

5. Nominal power: $P_N = 3 R'_2 \left(\frac{1}{s_N} - 1 \right) I_{1N}^2 = 3 \cdot 2.4 \cdot 81.48^2 = 47.8 \text{ kW}$

Nominal torque: $T_N = \frac{P_N}{\omega_n} = \frac{47800}{2\pi \frac{1440}{60}} = 317 \text{ N.m}$

6. Total power in nominal conditions:

$$P_1 = P_N + 1200 \text{ W} + \underbrace{3 \cdot (0.1 + 0.1) \cdot 81.48^2}_{3 \cdot (R'_2 + R_1) (I'_2)^2} = 52983 \text{ W}$$

efficiency : $\eta = \frac{P_N}{P_1} = \frac{47800}{52983} \approx 90 \%$

#

7. 10. Full load current

$$I = \frac{P}{\sqrt{3} V \cos \phi} = \frac{2 \cdot 10^6}{\sqrt{3} \cdot 15 \cdot 10^3 \cdot 1} = 94.28 \text{ A}$$

$$\vec{I} = I \angle 0 = 94.28 \angle 0 \text{ A}$$

$$\rightarrow \text{f.e.m } \vec{E}_0 = \frac{15000}{\sqrt{3}} + (0.5 + j10) 94.28 \angle 0 = (8707 + j942.8) \text{ V}$$

$$E_x = \frac{8758 - 8660}{8660} = 1.13 \% \quad \left(\text{where } E = 8660 = \frac{15000}{\sqrt{3}} \right)$$

8. Full load current:
$$I = \frac{P}{\sqrt{3} V \cos \phi} = \frac{2 \cdot 10^6}{\sqrt{3} \cdot 15 \cdot 10^3 \cdot 0.9} = 104.8 \text{ A}$$

$$\vec{I} = 104.8 (0.9 - j0.436) \text{ A}$$

$$\vec{E}_0 = \frac{15000}{\sqrt{3}} \angle 0 + (0.5 + j10) 104.8 (0.9 - j0.436) = (9164 + j920) \text{ V}$$

$$E_x = \frac{9210 - 8660}{8660} = 6.35 \%$$

9. Full load current
$$\vec{I} = 104.8 (0.9 + j0.436) \text{ A}$$

$$\vec{E}_0 = \frac{15000}{\sqrt{3}} \angle 0 + (0.5 + j10) 104.8 (0.9 + j0.436) = (8250 + j966) \text{ V}$$

$$E_x = \frac{8307 - 8660}{8660} = -4.08 \%$$

10. The complex power of the three loads is:

$$\bar{S}_1 = 700 \angle 36.9^\circ = (560 + j 420) \text{ kVA}$$

$$\bar{S}_2 = 1000 \angle 60^\circ = (500 + j 866) \text{ kVA}$$

$$\bar{S}_3 = 800 \angle 25.8^\circ = (720 + j 349) \text{ kVA}$$

The Total power is:

$$\begin{aligned} \bar{S}_T &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = (1780 + j 1635) \\ &= 2417 \angle 42.57^\circ \text{ kVA} \end{aligned}$$

Since $\bar{S}_T = \sqrt{3} \bar{V}_L \bar{I}_L^*$ and $S_T = \sqrt{3} V_L I_L$

the line current is:
$$I_L = \frac{2417 \cdot 10^3}{\sqrt{3} \cdot 13.8 \cdot 10^3} = 101.1 \text{ A (rms)}$$

11. The combined power factor for the three loads is found for the expression

$$\cos \theta = \text{pf} = \frac{1780}{2417} = 0.7365 \text{ lagging}$$

12. The new complex power with power factor 0.92 lagging is

$$\begin{aligned} \bar{S}_{\text{new}} &= 1780 + j 1780 \tan(23.07^\circ), \quad \text{where } \cos(23.07^\circ) = 0.92 \\ &= (1780 + j 758.28) \text{ kVA} \end{aligned}$$

The reactive power of the capacitor is: $\bar{S}_{\text{cap}} = j Q_C = \bar{S}_{\text{new}} - \bar{S}_T$

Assuming $V_{\text{rms}} = 15000/\sqrt{3}$ we obtain: $\bar{S}_{\text{cap}} = -j 876.72 \text{ kVA}$

$$j \omega C V_{\text{rms}}^2 = \frac{-j 876.72}{3} \Rightarrow C = 12.2 \mu\text{F} \quad \#$$