



# Per-unit System

## ELECTRICAL ENERGY SYSTEMS (EEEN20090)

Prof. Federico Milano

Email: [federico.milano@ucd.ie](mailto:federico.milano@ucd.ie)

Tel.: 01 716 1844

Room 157a – Engineering and Materials Science Centre

School of Electrical & Electronic Engineering

University College Dublin

Dublin, Ireland



## Per-unit System - I

- The per-unit system is widely used in power system analysis and simulation.
- It consists of a set of **BASES** with respect to which actual quantities are referred:

$$\text{per-unit value} = \frac{\text{actual value}}{\text{base value}}$$

- We need, thus, to choose a meaningful and complete set of base values for the electrical system.



## Per-unit System- II

- We just need 3 quantities:
  - $S_{\text{base}} = S_b$  [MVA]
  - $V_{\text{base}} = V_b$  [kV]
  - $f_{\text{base}} = f_b$  [kV]
- All other bases can be obtained from the quantities above.



## Per-unit System - III

- Current base:
  - Single-phase system:

$$I_b = \frac{S_b}{V_b} \quad [\text{kA}]$$

- Three-phase system:

$$I_b = \frac{S_b}{\sqrt{3}V_b} \quad [\text{kA}]$$

- Impedance base:
  - Both single and three-phase systems:

$$Z_b = \frac{V_b}{I_b^2} \quad [\Omega]$$

## Example 1

- Let's consider the following data:
  - $S_b = 100$  MVA
  - $V_b = 10$  kV
  - $x = 0.8$  pu with respect to  $S_b$  and  $V_b$ .
- What is the absolute value of the reactance in  $\Omega$ ?
- Solution:

$$X = x \cdot X_b = x \cdot \frac{V_b^2}{S_b} = 0.8 \cdot \frac{10^2}{100} = 0.8 \Omega$$

## Example 2

- Let's consider a transformer with following parameters and nominal values:

$$S_N = 700 \text{ MVA}, \quad V_{N1}/V_{N2} = 10\text{kV}/100\text{KV}, \quad V_{sc\%} = 10\%$$

- Determine the short-circuit impedance reduced to the primary and the secondary windings:

$$Z_{sc(1)} = V_{sc\%} \cdot \frac{V_{N1}^2}{S_N} = 0.1 \cdot \frac{10^2}{700} = 0.0143 \Omega$$

$$Z_{sc(2)} = V_{sc\%} \cdot \frac{V_{N2}^2}{S_N} = 0.1 \cdot \frac{100^2}{700} = 1.43 \Omega$$

- Note that the per-unit value of the short-circuit impedance of the transformer is  $\frac{1}{100} V_{sc\%}$  if we choose as bases the nominal quantities of the transformer.

## Example 2

- Note also that the per-unit value of the impedance is the same independently from the side of the transformer.
- In fact, let:
  - $Z_{b1} = \frac{V_{b1}^2}{S_b} = \frac{V_{N1}^2}{S_N}$
  - $Z_{b2} = \frac{V_{b2}^2}{S_b} = \frac{V_{N2}^2}{S_N}$
  - $z_{pu(1)}$  = per unit value reduced to the primary winding
  - $z_{pu(2)}$  = per unit value reduced to the secondary winding

## Example 2

- Then:


$$\begin{aligned} Z_{sc(1)} &= Z_{sc(2)} \frac{N_1^2}{N_2^2} \\ \Rightarrow z_{pu(1)} &= Z_{sc(1)} \frac{1}{Z_{b1}} = Z_{sc(1)} \frac{S_b}{V_{b1}^2} \\ &= Z_{sc(2)} \frac{N_1^2}{N_2^2} \frac{S_b}{V_{b1}^2} = Z_{sc(2)} \frac{S_b}{V_{b1}^2 \frac{N_1^2}{N_2^2}} \\ &= Z_{sc(2)} \frac{S_b}{V_{b2}^2} = Z_{sc(2)} \frac{1}{Z_{b2}} = z_{pu(2)} \end{aligned}$$

- Hence, if we choose as voltage bases the nominal voltages of the transformers, transformers can be modelled simply as impedances when using the per-unit system.



## Example 3


- Consider the following system:

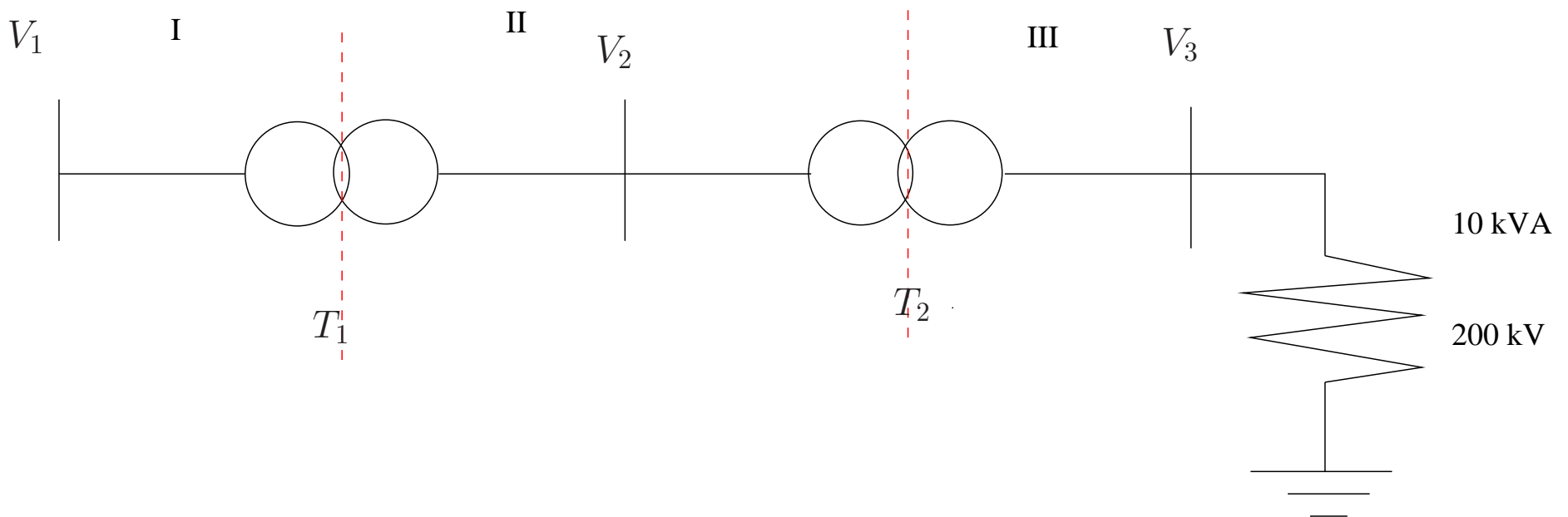

- The data of the transformers are:
  - $T_1$  : 10 kVA, 100V / 400V ,  $V_{sc\%} = 10\%$
  - $T_2$  : 10 kVA, 400V / 200V ,  $V_{sc\%} = 15\%$
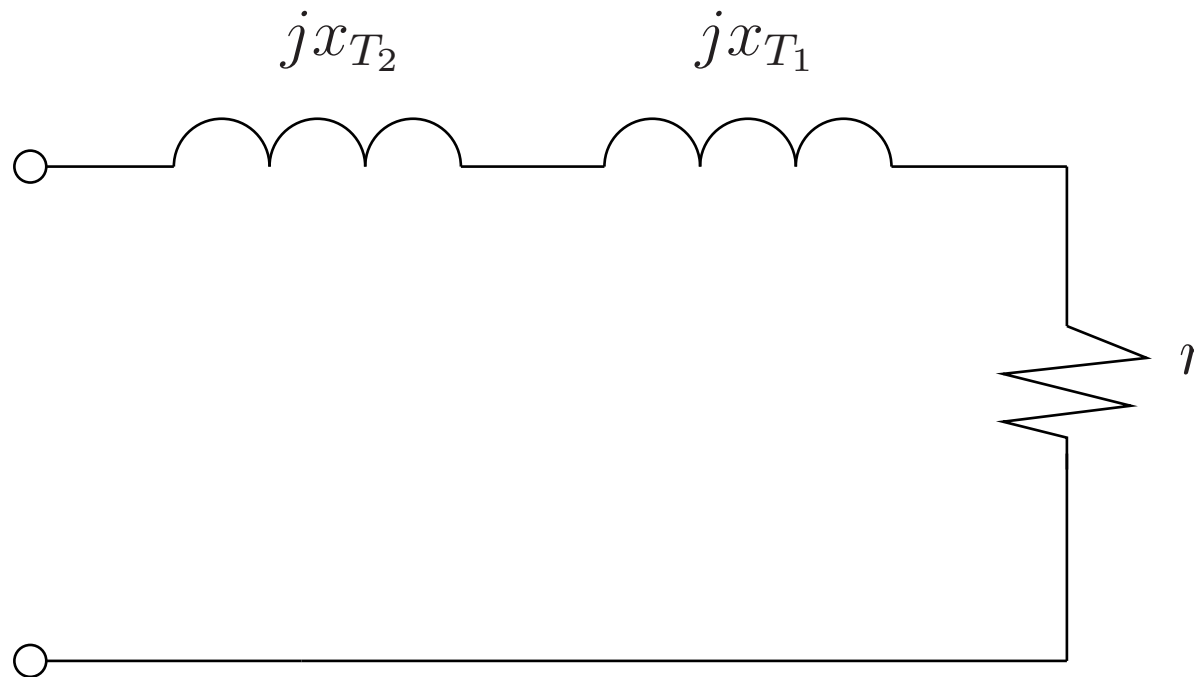
## Example 3

- Determine  $V_1$  such that  $V_3 = 200$  V on the resistance.
- Equivalent circuit in pu:



## Example 3

- First step: choose the bases.
  - $S_b = 10 \text{ kVA}$  → unique base for all regions.
- Regions are defined by transformers:
  - $V_{b1} = 100 \text{ V}$  → region I
  - $V_{b2} = 400 \text{ V}$  → region II
  - $V_{b3} = 200 \text{ V}$  → region III
- Equivalent resistance of the load:

$$R = \frac{V_3^2}{P} = \frac{200^2}{10^4} = 4 \Omega$$

## Example 3

- The impedance base for region III is:

$$Z_{b_{III}} = \frac{V_{b_{III}}^2}{S_b} = \frac{200^2}{10^4} = 4 \Omega$$

- Hence:

$$r(\text{pu}) = \frac{R}{Z_{b_{III}}} = \frac{4}{4} = 1 \text{ pu}$$

- Transformer reactances:


$$x_{T_2} = 0.15 \text{ pu}$$

$$x_{T_1} = 0.1 \text{ pu}$$

- The values of  $x_{T_1}$  and  $x_{T_2}$  are the same as short-circuit voltage as the bases of the transformers nominal quantities.

### Example 3

- The resulting circuit is:

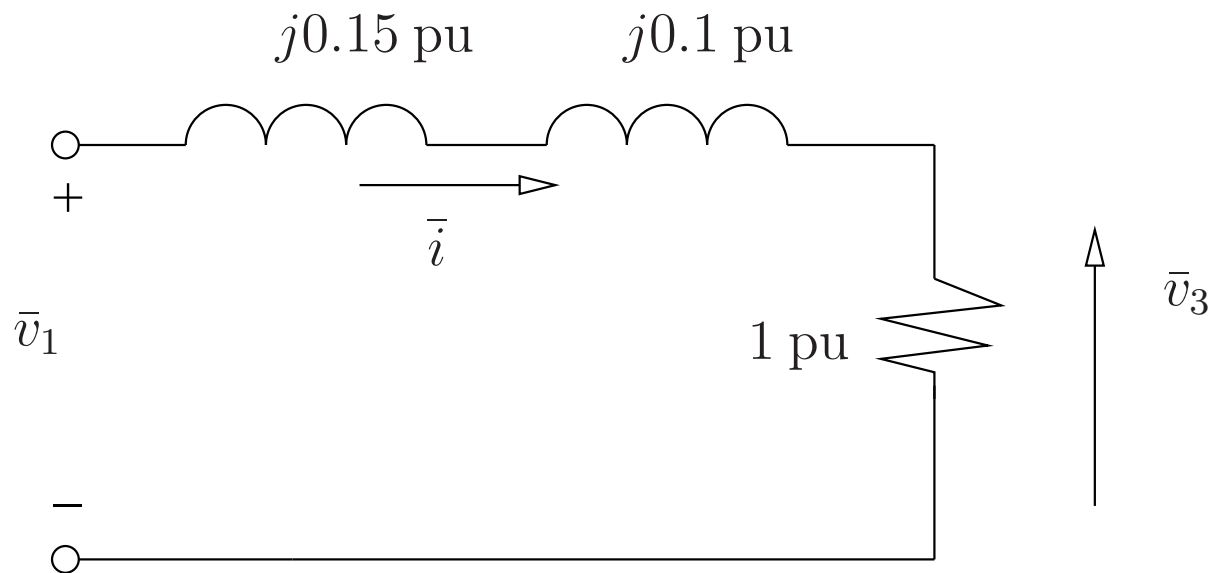

### Example 3

- We assume  $\angle \bar{v}_3 = 0$ , i.e, phase reference.

$$\bar{v}_3 = \frac{200}{v_{b_{III}}} = \frac{200}{200} = 1 \text{ pu} \bar{v}_1 = \bar{v}_3 + j(x_{T_1} + x_{T_2})\bar{i} = \frac{\bar{v}_3}{r} = 1 \text{ pu}$$

- Hence,

$$\bar{v}_1 = (1 + j0.25) \text{ pu}$$



## Example 4 - I

- A 21 MW load at 4 kV and 60 Hz is made of:
  - An inductive impedance load with  $G = 0.06047$ ,  $B = -0.03530$ .
  - An aggregated induction motor model with  $r_1 = 0.07825$ ,  $x_1 = 0.8320$ ,  $r'_2 = 0.1055$ ,  $x'_2 = 0.8320$ ,  $x_\mu = 16.48$ .
  - This data is all in pu on a 100 MVA, 4 kV base.

## Example 4 - II

- The  $Z$  load model is then:

$$\begin{aligned}P_L &= \frac{21 \text{ MW}}{100 \text{ MVA}} = 0.21 \\ &= P_Z + P_{IM}\end{aligned}$$

$$P_Z = V_L^2 G = 0.06$$

$$\Rightarrow P_{IM} = 0.15$$



### Example 4 - III

$$\begin{aligned}
 Z_{IM} &= r_1 + jx_1 + \frac{jx_\mu(r'_2/\sigma + jx'_2)}{r'_2/\sigma + j(x_\mu + x'_2)} \\
 &= 0.07825 + j0.832 + \frac{-13.7114 + j1.7386/\sigma}{0.1055/\sigma + j17.312} \\
 &= \left( 0.07825 + \frac{28.652/\sigma}{0.01113\sigma^2 + 299.71} \right) \\
 &\quad + j \left( 0.832 + \frac{0.18342/\sigma^2 + 237.37}{0.01113/\sigma^2 + 299.71} \right) \\
 &= \frac{(0.00087/\sigma^2 + 28.652/\sigma + 23.452) + j(0.19628/\sigma^2 + 486.73)}{0.01113/\sigma^2 + 299.71}
 \end{aligned}$$

## Example 4 - IV

$$P_{IM} = V_L^2 G_{IM} = G_{IM}$$

$$0.15 = \frac{(0.01113/\sigma^2 + 299.71)(0.00087/\sigma^2 + 28.652/\sigma + 23.452)}{(0.00087/\sigma^2 + 28.652/\sigma + 23.452)^2 + (0.19628/\sigma^2 + 486.73)^2}$$

$$\Rightarrow \sigma = 0.0191 \quad (\text{by trial-and-error})$$

$$\Rightarrow Z_{IM} = 4.6221 + j3.0742$$

$$Y_L = (G + jB) + \frac{1}{Z_{IM}}$$

$$Z_L = \frac{1}{Y_L} = 3.3654 + j2.1597$$