

# Worked Problem on Per Unit System

EEEN20090 – Electrical Energy Systems

## Problem 1

Consider the three-phases system shown in Figure 1:

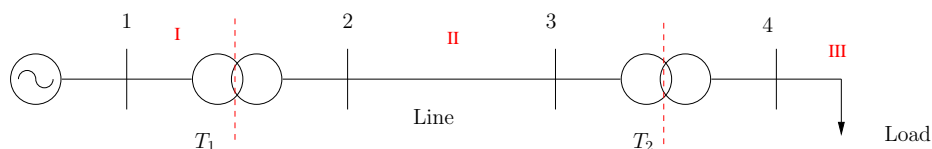


Figure 1

The data of the system are as follows:

$T_1$ : 50 MVA, 11 kV/ 132 kV,  $V_{sc\%} = 10 \%$

Line:  $X_L = 100 \Omega$

$T_2$ : 50 MVA, 132 kV/ 33 kV,  $V_{sc\%} = 12 \%$

Load: 50 MW,  $\cos \varphi = 0.8$

- Determine the voltage at bus 1 assuming that the voltage at bus 4 is  $V_4 = 30$  kV. Use  $S_b = 50$  MVA.
- Determine per-unit values of the equivalent circuit using as power base  $S_b = 100$  MVA.
- Determine per-unit values of the equivalent circuit using as voltage base for region III  $V_{b_{III}} = 30$  kV.
- Check that  $V_1$  in kV is the same for the three cases above.

## Solution of Problem 1

- a. Let's determine the equivalent circuit using the per-unit system.

Choose the bases first:

$$S_b = 50 \text{ MVA}$$

$$V_{b_I} = 11 \text{ kV}$$

$$V_{b_{II}} = 132 \text{ kV}$$

$$V_{b_{III}} = 33 \text{ kV}$$

$$Z_{b_{II}} = \frac{V_{b_{III}}^2}{S_b} = \frac{132^2}{50} = 348 \ \Omega$$

$$I_{b_{III}} = \frac{S_b}{\sqrt{3}V_{b_{III}}} = 0.875 \text{ kA}$$

Per-unit quantities:

$$x_{T_1} = 0.1 \text{ pu}$$

$$x_{T_2} = 0.12 \text{ pu}$$

$$x_L = \frac{100}{Z_{b_{II}}} = \frac{100}{348} = 0.287 \text{ pu}$$

$$v_4 = \frac{V_4}{V_{b_{III}}} = \frac{30}{33} = 0.91 \text{ pu}$$

Let  $\bar{v}_4$  be the phase reference:  $\bar{v}_4 = 0.91\angle 0$ .

The current in the circuit is:

$$I_L = \frac{P_L}{\sqrt{3}V_4 \cos \varphi} = \frac{50 \cdot 10^6}{\sqrt{3} \cdot 30 \cdot 10^3 \cdot 0.8} = 1.2 \text{ kA}$$

which, in per-unit, is:

$$i_L = \frac{I_L}{I_{b_{III}}} = \frac{1.2}{0.875} = 1.37 \text{ pu}$$

Since  $\bar{v}_4$  is the phase reference, we have:

$$\bar{i}_L = c = i_c(0.8 - j0.6) = (1.096 - j0.822) \text{ pu}$$

Finally:

$$\begin{aligned} \bar{v}_1 &= \bar{v}_4 + j(x_{T_1} + x_{T_2} + x_L)\bar{i}_c \\ &= 0.91 + j(0.1 + 0.12 + 0.287)(1.096 - j0.822) \\ &= (1.33 + j0.555) \text{ pu} = (1.44\angle 0.395 \text{ rad}) \text{ pu} \\ \Rightarrow V_1 &= |\bar{v}_1| \cdot V_{b_I} = 1.44 \cdot 11 = 15.84 \text{ kV} \end{aligned}$$

Note that the voltage drop is 44%!

b. Bases:

$$S_b = 100 \text{ MVA}$$

$$V_{b_I} = 11 \text{ kV}$$

$$V_{b_{II}} = 132 \text{ kV}$$

$$V_{b_{III}} = 33 \text{ kV}$$

$$Z_{b_{II}} = \frac{V_{b_{III}}^2}{S_b} = \frac{132^2}{100} = 174 \ \Omega$$

$$I_{b_{III}} = \frac{S_b}{\sqrt{3}V_{b_{III}}} = 1.75 \text{ kA}$$

System parameters, current and voltage on the load:

$$x_{T_1} = 0.1 \frac{S_b}{S_{N_1}} = 0.1 \frac{100}{50} = 0.2 \text{ pu}$$

$$x_{T_2} = 0.12 \frac{S_b}{S_{N_2}} = 0.12 \frac{100}{50} = 0.24 \text{ pu}$$

$$x_L = \frac{100}{174} = 0.575 \text{ pu}$$

$$i_L = \frac{1.2}{1.75} = 0.685 \text{ pu}$$

$$v_4 = \frac{30}{33} = 0.91 \text{ pu}$$

c. Bases:

$$S_b = 50 \text{ MVA}$$

$$V_{b_I} = 11 \frac{132}{33} \frac{30}{132} = 10 \text{ kV}$$

$$V_{b_{II}} = 132 \frac{30}{33} = 120 \text{ kV}$$

$$V_{b_{III}} = 30 \text{ kV}$$

$$Z_{b_{II}} = \frac{V_{b_{III}}^2}{S_b} = 288 \ \Omega$$

$$I_{b_{III}} = \frac{S_b}{\sqrt{3}V_{b_{III}}} = 0.96 \text{ kA}$$

System parameters, current and voltage on the load:

$$x_{T_1} = 0.1 \frac{V_{N_1}^2}{S_N} \frac{S_b}{V_{b_I}^2} = 0.1 \frac{11^2}{50} \frac{50}{10^2} = 0.121 \text{ pu}$$

$$x_{T_2} = 0.12 \frac{V_{N_1}^2}{S_N} \frac{S_b}{V_{b_{II}}^2} = 0.12 \frac{132^2}{50} \frac{50}{120^2} = 0.145 \text{ pu}$$

$$x_L = \frac{100}{Z_{b_{II}}} = \frac{100}{288} = 0.347 \text{ pu}$$

$$v_4 = \frac{30}{V_{b_{III}}} = \frac{30}{30} = 1 \text{ pu}$$

$$i_L = \frac{1.2}{I_{b_{III}}} = \frac{1.2}{0.96} = 1.25 \text{ pu}$$