

# Proposed Problems on Phasors and AC Circuits

## EEEN20090 – Electric Energy Systems

1. Find the amplitude, phase, period, frequency and angular frequency of the sinusoid  $v(t) = 12 \cos(314t + 12^\circ)$  V.
2. Calculate the phase angle between  $v_1(t) = -5 \cos(\omega t + 45^\circ)$  V and  $v_2(t) = 12 \sin(\omega t - 15^\circ)$  V State which sinusoid is leading.
3. Calculate the phase angle bw.  $v_1$  and  $v_2$  and sketch the phasor diagram.  $v_1 = -10 \cos(\omega t + 50^\circ)$ ,  $v_2 = 12 \sin(\omega t - 10^\circ)$ .
4. Calculate the phase angle bw.  $i_1$  and  $i_2$  and sketch the phasor diagram.  $i_1(t) = -4 \sin(377t + 25^\circ)$ ,  $i_2(t) = 5 \cos(377t - 40^\circ)$ .
5. Evaluate these complex numbers:

$$\sqrt[3]{25e^{-j45^\circ} + 12e^{j30^\circ}}, \quad \frac{10e^{-j30^\circ} + (3 - j3)}{(2 + j4)(3 - j5)^*}.$$

6. Evaluate the following complex numbers:

$$\begin{aligned} & [(5 - j2)(-1 + j4) - 5e^{j60^\circ}]^* \\ & \frac{10 + j5 + 3e^{j40^\circ}}{-3 + j4} + 10e^{j30^\circ} + j5 \end{aligned}$$

7. Transform these sinusoids to phasors:

$$\begin{aligned} v &= -24 \sin(314t + 63^\circ) \text{ V} \\ i &= 0.6 \cos(314t - 15^\circ) \text{ A} \end{aligned}$$

8. Find the sinusoids represented by these phasors:

$$\begin{aligned} \bar{V} &= j3e^{-j35^\circ} \\ \bar{I} &= -3 + j4 \end{aligned}$$


9. Using the phasor approach, determine the current  $i(t)$  in a circuit described by the integro-differential equation.

$$i + 2 \int i dt - 3 \frac{di}{dt} = 4 \cos(5t + 75^\circ) \text{ A}$$


10. Find the sum of the following currents and sketch the phasor diagram.

$$\begin{aligned} i_1 &= 4 \cos(\omega t + 30^\circ) \text{ A} \\ i_2 &= 5 \sin(\omega t - 206^\circ) \text{ A} \end{aligned}$$

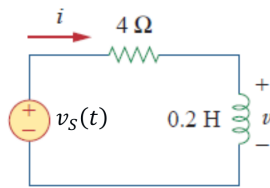
11. The voltage  $v = 24 \cos(314t + 45^\circ)$  V is applied to a 100 mH inductor. Find the steady-state current through the inductor.
12. The voltage  $v = 6 \cos(100t - 30^\circ)$  V is applied to a 50  $\mu$ F capacitor. Calculate the current through the capacitor and sketch the phasor diagram.
13. Find  $v(t)$  and  $i(t)$  in the circuit below assuming  $v_s(t) = 5 \sin(10t)$ .



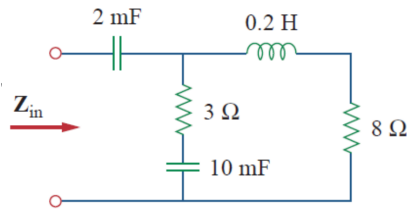14. Find  $\bar{Z}_{\text{in}}$  in the circuit below assuming  $\omega = 50 \text{ rad/s}$ .



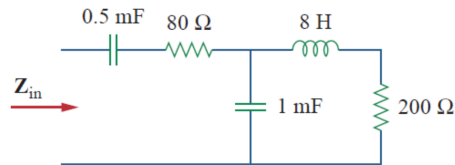15. Find  $\bar{Z}_{\text{in}}$  in the circuit below assuming  $\omega = 10 \text{ rad/s}$ .



16. Find  $v_0(t)$  in the circuit below assuming  $v_s(t) = 20 \cos(4t - 15^\circ)$  V.

