

Worked Problems on Three-Phase Systems

EEEN20090 – Electrical Energy Systems

Problem 1

A 3-phase inductive load is connected in Δ and in parallel with a capacitor bank. The load current is K and the phase-to-phase voltage is $\frac{1}{K}$. Determine the value of the line current of the capacitor bank such that the overall power factor is unity.

Problem 2

The voltages of the three-phase system shown in Figure are:

$$\bar{E}_a = 1 \text{ V}, \quad \bar{E}_b = -1 \text{ V}, \quad \bar{E}_c = j1 \text{ V}.$$

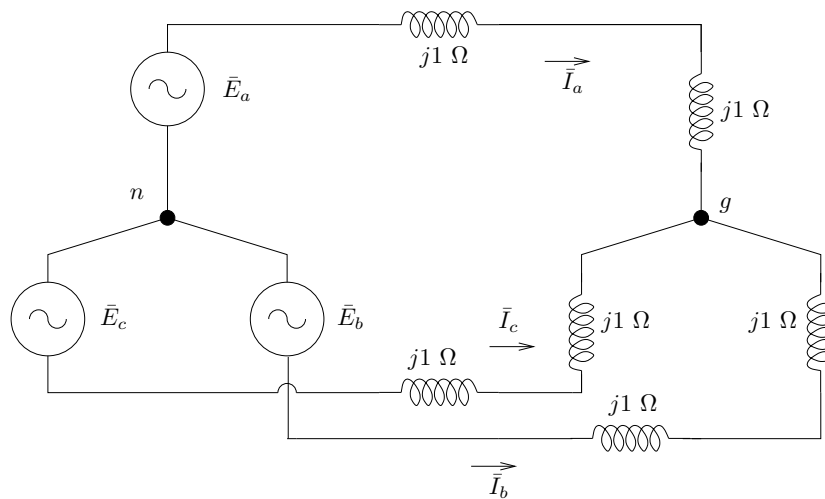


Figure 1

Determine:

- The currents \bar{I}_a , \bar{I}_b and \bar{I}_c .
- The voltage \bar{V}_{ng} .

Problem 3

A 3-phase cable *A* feeds a 1000 kW, 6.6 kV load with power factor $\cos \varphi = 0.8$ lagging. Another cable *B* is connected in parallel with cable *A*. The impedance of cable *B* is $(3 + j4)\Omega$ per phase. When connected in parallel with cable *B*, cable *A* delivers 600 kW and its current is 68 A. Determine the impedance of cable *A*.

Problem 4

Consider the symmetrical, balanced 3-phase system shown in Figure .

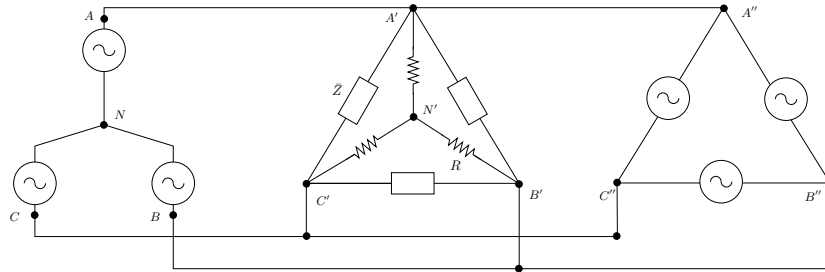


Figure 2

$$V = 220V, R = 100\Omega, \bar{V}_{C'A''} = \sqrt{3}V \angle 30^\circ, \bar{V}_{CN} = V \angle 0^\circ$$

The impedance \bar{Z} is capacitive and, at nominal voltage (400 V) consumes 2400 VAR.

Determine:

- The total load power consumed by the parallel of R and \bar{Z} .
- The magnitude of current $I_{B'A'}$.

Solution of Problem 1

Let \bar{S}_L be the power of the load and \bar{S}_C the power of the capacitor bank. Then:

$$\begin{aligned}\bar{S}_L &= \sqrt{3}K \frac{1}{K} \angle \varphi \\ \bar{S}_C &= -\frac{\sqrt{3}}{K} I_C \angle 90^\circ\end{aligned}$$

The total power consumed by the load and the capacitors is:

$$\bar{S}_T = \sqrt{3} \cos \varphi + j\sqrt{3} \sin \varphi - j\frac{\sqrt{3}I_C}{K}$$

If we impose that $\cos \varphi_T = 1$, then the imaginary part of \bar{S}_T is zero:

$$\text{Im}\{\bar{S}_T\} = \sqrt{3} \sin \varphi - \frac{\sqrt{3}I_C}{K} \text{Im}\bar{S}_T = 0 \Rightarrow I_C = K \sin \varphi$$

Solution of Problem 2

a. KVL gives:

$$\begin{cases} \bar{E}_a - jX\bar{I}_a + jX\bar{I}_b - \bar{E}_b = 0 \\ \bar{E}_a - jX\bar{I}_a + jX\bar{I}_c - \bar{E}_c = 0 \end{cases}$$

where $X = 2 \Omega$. Then, from KCL: $\bar{I}_a + \bar{I}_b + \bar{I}_c = 0$. Hence:

$$\begin{bmatrix} -jX & jX & 0 \\ -jX & 0 & jX \\ 1 & 1 & 1 \end{bmatrix} \cdot \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \begin{bmatrix} \bar{E}_b - \bar{E}_a \\ \bar{E}_c - \bar{E}_a \\ 0 \end{bmatrix}$$

From where we can obtain:

$$\begin{cases} \bar{I}_a = -0.1667 - j0.5 \text{ A} \\ \bar{I}_b = -0.1667 + j0.5 \text{ A} \\ \bar{I}_c = 0.3333 \text{ A} \end{cases}$$

b. The voltage \bar{V}_{ng} is obtained as:

$$\bar{V}_{ng} = jX\bar{I}_a - \bar{E}_a = jX(-0.1667 - j0.5) - 1 = -j0.3333 \text{ V}$$

Note: An alternative solution is based on the Milligan's theorem, as follows:

$$\begin{aligned}\bar{V}_{ng} = -\bar{V}_{gn} &= -\frac{\bar{Y}_a\bar{E}_a + \bar{Y}_b\bar{E}_b + \bar{Y}_c\bar{E}_c}{\bar{Y}_a + \bar{Y}_b + \bar{Y}_c + \bar{Y}_{ng}} \\ &= -\frac{\bar{Y} \cdot (\bar{E}_a + \bar{E}_b + \bar{E}_c)}{3\bar{Y}} \\ &= -\frac{1}{3}(\bar{E}_a + \bar{E}_b + \bar{E}_c) = -j0.3333 \text{ V} ,\end{aligned}$$

where it has been imposed that $\bar{Y}_{ng} = 0$ and $\bar{Y} = \bar{Y}_a = \bar{Y}_b = \bar{Y}_c$. Then currents can be deduced from the following expressions:

$$0 = \bar{E}_a - jX\bar{I}_a + \bar{V}_{gn}$$

$$0 = \bar{E}_b - jX\bar{I}_b + \bar{V}_{gn}$$

$$0 = \bar{E}_c - jX\bar{I}_c + \bar{V}_{gn} .$$

Solution of Problem 3

The data of the problem lead to the following equations:

$$I_{AR} + jI_{AI} + I_{BR} + jI_{BI} = \frac{P - jQ}{\frac{3}{\sqrt{3}}V} \quad (1)$$

$$\bar{z}_A(I_{AR} + jI_{AI}) = \bar{z}_B(I_{BR} + jI_{BI}) \quad (2)$$

$$\sqrt{(I_{AR}^2 + I_{AI}^2)} = 68 \text{ A} \quad (3)$$

$$I_{AR} = \frac{600}{\frac{3}{\sqrt{3}}V} \text{ A} \quad (4)$$

where

$$\bar{I}_A = I_{AR} + jI_{AI}$$

$$\bar{I}_B = I_{BR} + jI_{BI}$$

$$V = 6.6 \text{ kV}$$

$$P + jQ = (1000 + j750) \text{ kVA}$$

Equation (1) imposes that the two cables when connected in parallel feed the load $P + jQ$. Equation (2) imposes that the voltage drop on the two cables when connected in parallel is the same. Equation (3) imposes the magnitude of the current in cable A . Equation (4) imposes the active power provided by cable A when connected in parallel with cable B . Equations (1)-(4) provide 6 conditions for 6 unknowns (I_{AR} , I_{AI} , I_{BR} , I_{BI} , $\bar{z}_A = R_A + jX_A$), hence the problem is well-posed and can be solved.

The resulting values are:

$$I_{AR} = 52.5 \text{ A}$$

$$I_{AI} = -43.2 \text{ A}$$

$$I_{BR} = 35.0 \text{ A}$$

$$I_{BI} = -22.4 \text{ A}$$

$$\bar{Z}_A = (1.53 + j2.65) \Omega$$

Solution of Problem 4

The equivalent single-phase circuit is shown in Figure 3, where:

$$\bar{Z} = -j \frac{V_N^2}{Q_N} = -j 3 \frac{400^2}{2400} = -j 200 \Omega$$

$$\begin{aligned} \bar{V}_{AN} &= V (\angle \bar{V}_{CN} - \angle 120^\circ) \\ &= 220 \angle -120^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} \bar{V}_{A''N''} &= V (\angle \bar{V}_{C''A''} - \angle 150^\circ) \\ &= V \angle (30^\circ - 150^\circ) \\ &= 220 \angle -120^\circ \text{ V} \end{aligned}$$

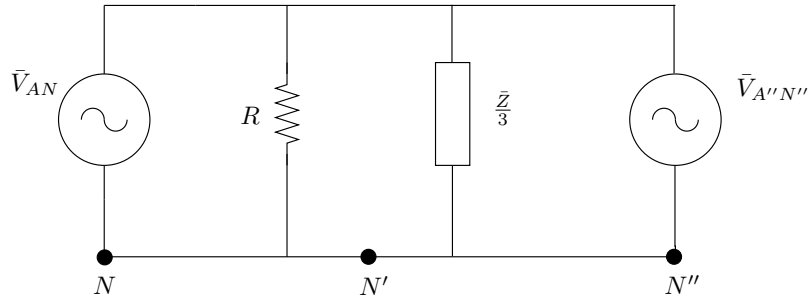


Figure 3

- a. The total power of the parallel of \bar{z} and R is:

$$\begin{aligned} \bar{S} &= 3 \frac{V^2}{R} - j 3 \frac{V^2}{\frac{|z|}{3}} \\ &= 3 \frac{220^2}{100} - j 3 \frac{220^2}{\frac{200}{3}} \\ &= (1452 - j 2178) \text{ VA} \end{aligned}$$

- b. The magnitude of current $I_{B'A'}$ is:

$$\begin{aligned} \bar{I}_{B'A'} &= \left[\frac{1}{\sqrt{3}} \frac{V \angle -120^\circ}{\frac{2}{3} \angle -90^\circ} \angle 30^\circ \angle 180^\circ \right] \\ &= \frac{3 \cdot 220}{\sqrt{3} \cdot 200} (\angle -120^\circ + 90^\circ + 30^\circ + 180^\circ) \\ &= 1.9 \angle 180^\circ \text{ A} \end{aligned}$$